

CURRENT ELECTRICITY - 2RESISTANCE, RESISTIVITY & OHM'S LAWCurrent Electricity - 2

Factors affecting resistance \Rightarrow The resistance R of a metallic conductor is (i) directly proportional to length l
(ii) inversely to its area of cross-section A

i.e. $R \propto l$; $R \propto \frac{1}{A} \Rightarrow R = \rho \frac{l}{A}$ where ρ is a constant called resistivity of the material of the conductor.

The value of ρ is independent of shape and size but depends on the temperature in addition to the nature of the material. For $l = 1\text{m}$; $A = 1\text{sq. m}$; $\rho = R$

Hence resistivity of the material of a conductor is numerically equal to the resistance of a 1m long conductor with a uniform area of cross-section 1sq.m. Its SI unit is $\Omega\text{-m}$. Its value varies from very low for metals (e.g. $1.6 \times 10^{-8} \Omega\text{m}$) for silver to very high (e.g. 10^{13} to 10^{16}) for rubber.

Ohm's Law. [Recall $I = \frac{n e^2 A \tau}{m} E$ for a conductor (Current E and I)]
For a conductor $I = \frac{n e^2 A \tau}{m} E = \frac{n e^2 A \tau}{m} \frac{V}{l}$ [As $E = \frac{V}{l}$]

$\therefore \frac{V}{I} = \left(\frac{m}{e^2 n \tau} \right) \frac{l}{A}$. For a conductor of given length and area of cross-section, all the terms on RHS are constant at a given temperature (τ varies with temperature decreasing with increasing temperature)

Hence $\frac{V}{I} = \text{constant}$ which is Ohm's law.

Hence Ohm's law can be stated as under:

"For a conductor at a fixed temperature, the potential difference applied across its ends is directly proportional to the current passing through it."

VARIATION OF RESISTANCE WITH TEMPERATURE

Expression for resistance (We have $R = \frac{V}{I}$) defined as the measure of ability of a conductor to oppose the flow of current through itself. [Scalar with SI units ohm (Ω)].

Using $\frac{V}{I} = \frac{m \ell}{e^2 n \tau A}$ and $R = \frac{V}{I}$, we get

$$R = \frac{m \ell}{e^2 n \tau A} \text{ which is the required expression.}$$

Expression for resistivity Comparing $R = \rho \frac{\ell}{A}$ and $R = \left(\frac{m}{e^2 n \tau} \right) \frac{\ell}{A}$

we get $\rho = \frac{m}{e^2 n \tau}$

Effect of temp. on Resistance/resistivity

- (i) Conductors For a conductor; the resistance is caused by the collisions between the electrons as they ~~are~~ are in constant random thermal motion. At higher temperature; the random motion increases resulting in more frequent collisions lesser free time τ . Hence the resistance and resistivity of a conductor increase with rise in temperature. [for graphical representation of ρ vs τ see NCERT book]

Mathematically $R_t = R_0 [1 + \alpha t]$ where

R_t is resistance at $t^\circ\text{C}$; R_0 at 0°C and α is the temperature co-efficient of resistance. $\left[\alpha = \frac{R_t - R_0}{R_0 \cdot t} \right]$ defined as the increase in resistance per unit resistance per $^\circ\text{C}$ rise in temperature. (or per kelvin)

SI unit of α is K^{-1} .

ELECTRIC ENERGY AND POWER

(ii) In a semiconductor, as temperature increases, the bonds between atoms break up resulting in a sharp increase in the number of free charge carriers. (i.e. electrons and holes) increases. Hence the resistivity/resistance of semiconductors decreases with rise in temperature.

The temperature coefficient of resistance is positive for metals and negative for semiconductors.

Colour code for Carbon resistances; Resistances in series and parallel: Refer to book.

Electrical Energy and Power

A conductor of resistance R , subjected to a potential difference ' V ' shown in the figure allows a current ' I ' to pass through itself.

\therefore Charge transferred in ' t ' sec = $q = I \cdot t$.

Now Potential difference $V = \frac{\text{Work}}{\text{Charge}} = \frac{W}{q} \Rightarrow W = qV = V \cdot I \cdot t$.

This is a measure of the electrical energy consumed in the resistor in time ' t '.

$\therefore W = V I t$ or electrical energy consumed = $V I t = I^2 R t = \frac{V^2}{R} t$.

and Electrical power $P = \frac{W}{t} = V I = I^2 R = \frac{V^2}{R}$

SI unit of electric energy is joule (= Watt . 1 sec)


The practical unit of electric energy is kWh

with $1 \text{ kWh} = 3.6 \times 10^6 \text{ J}$.

EMF & INTERNAL RESISTANCEInternal Resistance ; EMF and Potential Difference of a cell

The resistance offered by the electrolyte of a cell during flow of current through itself is called internal resistance (r)

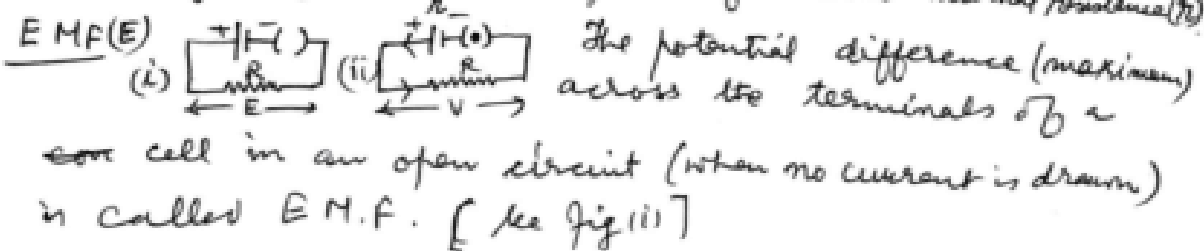The potential difference (maximum) across the terminals of a cell in an open circuit (when no current is drawn) is called E.M.F. [see fig (ii)]



The potential difference (V) between the poles of a cell in use when current is being drawn from it is called terminal potential difference.

Relation between E , V and r Consider a cell of emf ' E ' and internal resistance ' r ' used to drive a current ' I ' through an external resistance R .

Total resistance of the circuit = $(R + r)$.

$$\therefore E = I(R + r) = IR + Ir = V + Ir$$

$$\Rightarrow r = \frac{E - V}{I} = \left(\frac{E - V}{V/R} \right) = \left(\frac{E - V}{V} \right) R$$

The relation imply that $E > V$; $E = V$ if $I = 0$ or $R = \infty$

Note \rightarrow The potential difference V exceeds the EMF of a cell when it is being charged.

Sample Problem 1 \rightarrow A wire of resistance 50Ω is drawn out to double its original length. What will be its new (i) resistivity (ii) resistance? Give original resistivity x units.

Ans \rightarrow (i) Resistivity does not depend on shape/size. So it still remains x units

(ii) We have $R = \rho \frac{l}{A}$.

So $R' = \rho \frac{l'}{A'}$. For the wire volume remains unchanged

$$\therefore lA = l'A' \Rightarrow A' = A \cdot \frac{l}{l'} = A \cdot \frac{l}{2l} = \frac{A}{2} \quad [\because l' = 2l]$$

$$\therefore R' = \rho \frac{l'}{A'} = \frac{2l\rho}{A/2} = 4 \frac{\rho l}{A} = 4R = 4(5\Omega) = 20\Omega$$

Sample Problem 2 :- Calculate the conductivity of a material if a 3m long conductor with area of cross-section 0.2 mm^2 has a resistance of 2ohm.

Solution :- We have $R = \rho \frac{l}{A}$ or $\rho = \frac{RA}{l}$.

$$\therefore \text{Conductivity } \sigma = \frac{1}{\rho} = \frac{l}{RA} = \frac{3}{2 \times 0.2 \times 10^{-4}} = 7.5 \times 10^6 \text{ Sm}^{-1}$$


Sample Problem 3 :- Two lamps are marked 60W; 220V and 100W; 220V. Compare their resistances.

Solution We have $P = \frac{V^2}{R} \Rightarrow R = \frac{V^2}{P}$.

$$\therefore \frac{R_1}{R_2} = \frac{P_2}{P_1} \text{ or } \frac{R_{60W}}{R_{100W}} = \frac{100}{60} = \frac{5}{3}$$

Sample Problem 4 :- The V-I graph for a metallic wire at two different temperatures T_1 and T_2 is as shown in Fig. 77. Which of the two temperatures T_1 and T_2 is higher and why?

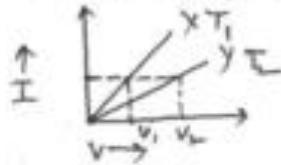Ans. If same current I is to be passed through the wires; X requires a potential difference V_1 and Y requires V_2 .



From the graph $V_2 > V_1 \Rightarrow R_Y > R_X$ or $T_2 > T_1$

Sample Problem 5 n identical resistances each of resistance R have resistance X when joined in series and Y when joined in parallel.

Calculate X/Y.

Solution :- In series; $X = R + R + \dots + R = nR$
 In parallel $\frac{1}{Y} = \frac{1}{R} + \frac{1}{R} + \dots + \frac{1}{R} \text{ (n times)} \Rightarrow \frac{1}{Y} = \frac{n}{R}$ or $Y = \frac{R}{n}$